

- You have **120 minutes** to answer the questions.
- Please write your **name** and **roll number** at appropriate places.
- Write the **key steps** of your solution of the problems in the space provided.
- You can solve the problems in the supplementary sheets provided. Please attach the same to this paper.

Name: _____ Roll number: _____

1. Mark the typical (approximate) power rating of the following devices: **2 marks**

(i) Ceiling Fan: (a) 10 W (b) ~~70 W~~ (c) 500 W (d) 5 kW. **(1)**

(ii) Air Conditioner: (a) 15 W (b) 150 W (c) ~~1.5 kW~~ (d) 5 kW. **(1)**

2. A three phase device has its nameplate rating as 50 Hz, 3 kW, 415 V. The voltage rating refers to: **1 mark**

(a) Line to line peak value (b) ~~Line to line rms value~~ (c) Line to neutral peak value (d) Line to neutral rms value. **(1)**

3. The currents in the three phases of a star-connected load are $I_a = 4\angle 30^\circ$ A, $I_b = 4\angle 170^\circ$ A and $I_c = 4\angle -10^\circ$ A. The current through the neutral is **1 mark**

(a) 0 A (b) ~~$4\angle 30^\circ$ A~~ (c) $2\sqrt{3}\angle 60^\circ$ A (d) $2\angle 120^\circ$ A. **(1)** $4\angle 30^\circ + 4\angle 170^\circ + 4\angle -10^\circ = 4\angle 30^\circ + 4\angle 170^\circ - 4\angle 170^\circ$

4. Typical range of 50 Hz current that induces some perception (tingling sensation) in a human being is approximately **1 mark**

(a) 1-5 μ A (b) ~~1-5 mA~~ (c) 1-5 A (d) 10-50 A **(1)**

5. For the circuit shown in Figure 1, find the current I_R . **3 marks**

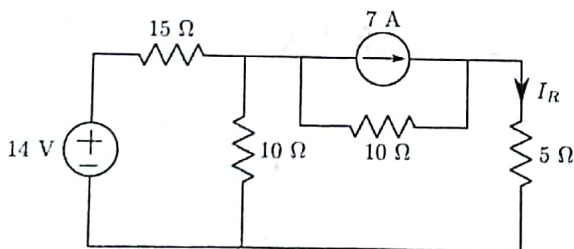


Figure 1: Circuit for Problem 5

Applying superposition,

$$I_{R1} = \frac{14}{15} \times \frac{6}{6+15} \text{ A}$$

$$= \frac{14}{15} \times \frac{6}{21} \text{ A}$$




$$= \frac{4}{15} \text{ A.}$$

$$I_{R2} = 7 \times \frac{10}{10+11} \text{ A}$$

$$= 7 \times \frac{10}{21} \text{ A}$$

$$= \frac{10}{3} \text{ A.}$$
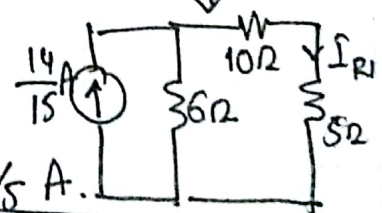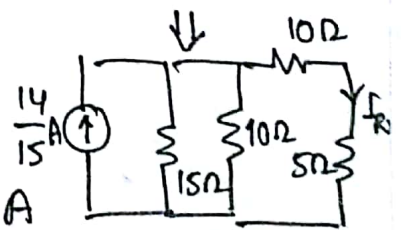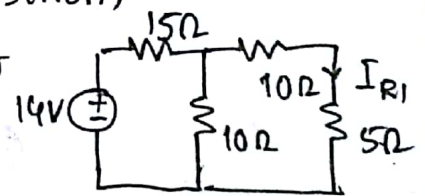
$$I_R = \frac{4}{15} + \frac{10}{3} = \frac{18}{5} \text{ A.}$$



6. For the circuit shown in Figure 2, find the steady state value of I .

3 marks


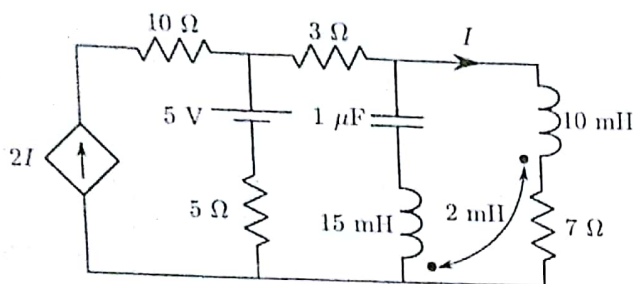


Figure 2: Circuit for Problem 6

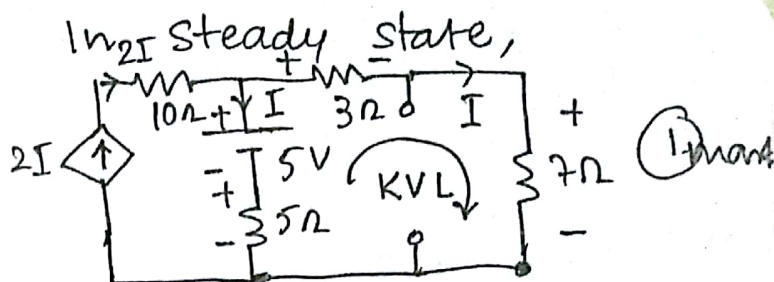

Applying KVL,

$$5I + 5 - 3I - 7I = 0 \quad (1 \text{ mark})$$

$$\text{or, } 5 = 5I \Rightarrow \boxed{I = 1 \text{ A}} \quad (1 \text{ mark})$$

7. A resistance R is connected to a linear network and the current flowing through it is I as shown in Figure 3. It is observed that for $R = 2 \Omega$, I is 5 A and for $R = 3 \Omega$, I is 4 A (all quantities are steady state values). Find the steady state value of I for $R = 8 \Omega$.

3 marks


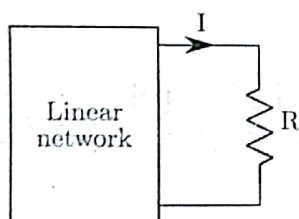


Figure 3: Circuit for Problem 7

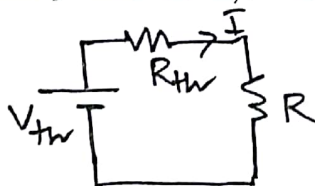

$$V_{th} = R_{th} \cdot I + R \cdot I$$

$$V_{th} - 5R_{th} = 10 \quad (1)$$

$$V_{th} - 4R_{th} = 12 \quad (2)$$

Putting in (1),

$$V_{th} = 10 + 5 \times 2 = 20 \text{ V} \quad (1 \text{ mark})$$

By (2) - (1),

$$R_{th} = 2 \quad (1 \text{ mark})$$

$$I = \frac{V_{th}}{R_{th} + R} = \frac{20}{2 + 8} = \boxed{2 \text{ A}} \quad (1 \text{ mark})$$

8. For a balanced three-phase load supplied by a balanced three-phase source, which of the following is/are true? (Tick the correct option(s))

1 mark

(a) Three-phase instantaneous power is constant

0.5 mark

(b) Per phase instantaneous power is constant

(c) Instantaneous power in all phases are equal to each other

(d) Reactive power in all phases are equal to each other. 0.5 mark.

Cont.

9. For the circuit shown in Figure 4, the switch S was at position 1 for a very long time (1 hour or so). At $t = 0$, the switch S is now connected to position 2.

(a) Find the expression of $i(t)$ for $t \geq 0$.

(b) If the capacitor voltage is $v_c(t)$, calculate $\frac{dv_c(t)}{dt}$ at $t = 0^+$.

4 marks

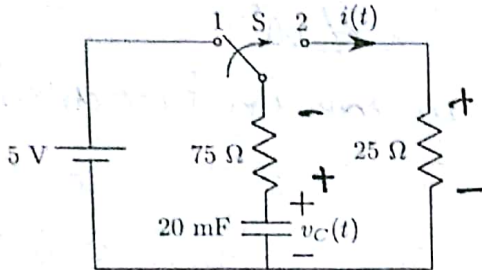


Figure 4: Circuit for Problem 9

Since it is at steady state,
 $v_c(0^-) = 5V$. — ① mark

At $t = 0$, switching is done.

$$i(t) = -C \frac{dv_c(t)}{dt}$$

$$v_c(t) - 100 i(t) = 0 \Rightarrow i(t) = \frac{v_c(t)}{100}$$

$$\therefore \frac{dv_c(t)}{dt} = -\frac{v_c(t)}{100 \cdot C} \Rightarrow \frac{dv_c}{dt} \bigg|_{0^+} = -\frac{5}{100 \times 20 \times 10^{-3}}$$

10. A series R-L-C circuit is excited by a DC voltage source of 10 V. Assuming zero initial conditions, tick the following which is/are true.

1 mark

- (a) For $R = 15 \Omega$, $L = 1 \text{ mH}$, $C = 40 \mu\text{F}$, response is non-oscillatory.
 (b) For $R = 15 \Omega$, $L = 1 \text{ mH}$, $C = 40 \mu\text{F}$, response is oscillatory.
 (c) For $R = 5 \Omega$, $L = 1 \text{ mH}$, $C = 40 \mu\text{F}$, response is non-oscillatory.
 (d) For $R = 5 \Omega$, $L = 1 \text{ mH}$, $C = 40 \mu\text{F}$, response is oscillatory.


$$\text{eigenvalues} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

11. Two single phase loads of power factors 0.8 (lag) and 0.9 (lag) respectively are connected in parallel. The overall power factor of the combined load is

1 mark

- (a) < 0.8 (lag) (b) between 0.8 (lag) and 0.9 (lag) (c) > 0.9 (lag) (d) indeterminate.

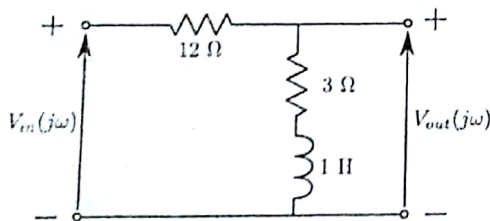12. Calculate the transfer function $\frac{V_{out}(j\omega)}{V_{in}(j\omega)}$ for the circuit shown in Figure 5, where ω is in rad/s. Find the gain and the phase shift of the transfer function at (i) $f = 0.2 \text{ Hz}$, (ii) $f = 2 \text{ Hz}$, (iii) $f = 20 \text{ Hz}$. Indicate the phase lead or lag appropriately. 4 marks



$$\frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{3 + j\omega \cdot 1}{3 + 12 + j\omega \cdot 1}$$

$$= \frac{3 + j\omega}{15 + j\omega}, \omega \text{ is in rad/s}$$


Figure 5: Circuit for Problem 12 $f = 0.2 \text{ Hz} \Rightarrow \omega = 1.2566 \text{ rad/s}$.

Frequency | Gain | Phase (lead)

13. For the circuit shown in Figure 6, the frequency of the voltage source $v_s(t)$ is 50 Hz. \bar{I}_1 and \bar{I}_2 are the phasor representations of $i_1(t)$ and $i_2(t)$ respectively and they are related as $\frac{\bar{I}_2}{\bar{I}_1} = 2\angle 30^\circ$. 5 marks


(a) Find the value of C .

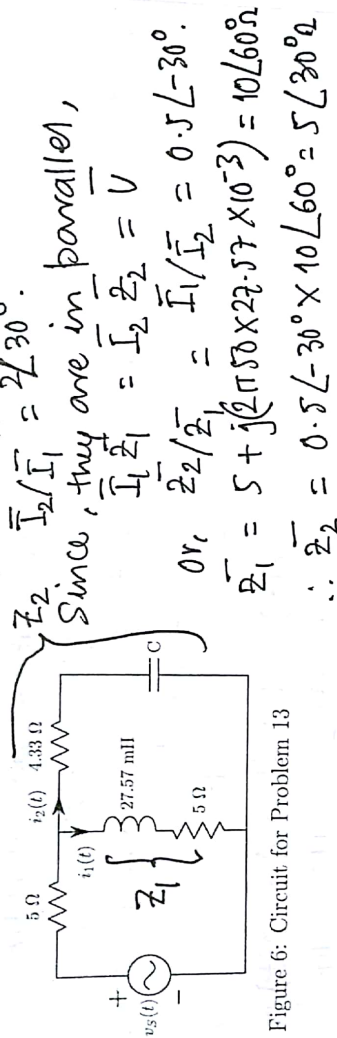(b) If $i_1(t) = 5 \sin(2\pi \times 50t)$, find the expression of $v_s(t)$.



Incorrect data.

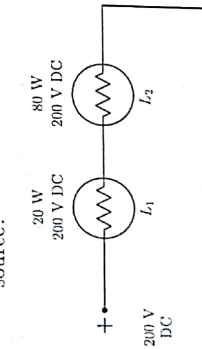14. Two lamps L_1 and L_2 are connected in series across a 200 V DC supply as shown in Figure 7. The ratings of L_1 and L_2 are (20 W, 200 V DC) and (80 W, 200 V DC) respectively. Which bulb glows brighter and what is the total power delivered by the source? 4 marks



In series, I is constant.

$$\therefore P_1 = I^2 R_1, P_2 = I^2 R_2.$$

Since $R_1 > R_2$, so $P_1 > P_2$.

L_1 glows brighter. — 1 mark.

Cont.

$$I = \frac{200}{2000 + 500} = 0.08 \text{ A.} \quad P = I^2 (R_1 + R_2) = 0.08^2 \times 2500 = 16 \text{ W.} \quad \text{— 1 mark}$$

$$P = \frac{V^2}{R} \quad L_1: R_1 = \frac{V^2}{P} = \frac{200^2}{20} = 2000 \Omega$$

$$L_2: R_2 = \frac{200^2}{80} = 500 \Omega.$$

1 mark.

15. The voltage $v(t)$ across a particular component and the current $i(t)$ through it are given as

$$v(t) = 5 - 10 \sin(2\pi \times 50t - 25^\circ) \text{ V.}$$

$$i(t) = 2 + k \sin(2\pi \times 50t + 35^\circ) \text{ A.}$$

Find k such that the average power dissipated in the component is zero. 2 marks

$$P_{dc} = 5 \times 2 = 10 \text{ W.} \quad \text{--- (0.5) marks}$$

$$P_{ac} = \frac{10 \times k}{2} \cos [35 - (180 - 25)] = 5k \cos (120) = -\frac{5k}{2}.$$

$$\therefore 10 - \frac{5k}{2} = 0 \Rightarrow \boxed{k = 4} \quad \text{(1) mark} \quad \text{(0.5) marks}$$

16. A balanced star-connected three phase load of impedance $Z = 10 \angle 30^\circ$ per phase is connected to a three phase voltage source given as

$$v_{an}(t) = \sqrt{2} \times 100 \sin(2\pi \times 50t) \text{ V}$$

$$v_{bn}(t) = \sqrt{2} \times 100 \sin\left(2\pi \times 50t - \frac{2\pi}{3}\right) \text{ V}$$

$$v_{cn}(t) = \sqrt{2} \times 100 \sin\left(2\pi \times 50t + \frac{2\pi}{3}\right) \text{ V.}$$

- (a) For $T = 0.02$ s, find the value of $\frac{\sqrt{3}}{T} \int_0^T (v_{bn}(t) - v_{cn}(t)) i_a(t) dt$, where $i_a(t)$ is the phase a line current.

- (b) Calculate the total reactive power absorbed by the load. 4 marks

$T = 0.02$ s is one complete cycle of 50 Hz.

$$\frac{1}{T} \int_0^T v_{bc}(t) i_a(t) dt = (V_{bc})_{rms} \cdot (I_a)_{rms} \cos \angle \begin{matrix} V_{bc} \\ I_a \end{matrix}$$

$$(V_{an})_{rms} = 100 \text{ V, } (V_{bc})_{rms} = \sqrt{3} \times 100 \text{ V.} \quad \text{--- (1) mark}$$

$$(i_a)_{rms} = \frac{(V_{an})_{rms}}{|Z|} = 10 \text{ A.} \quad \text{--- (1) mark.}$$

$$v_{bc}(t) = v_{bn}(t) - v_{cn}(t) = \sqrt{2} \times 100 \sqrt{3} \sin(\omega t - 90^\circ).$$

$$i_a(t) = v_{an}(t) / |Z| = \sqrt{2} \times \frac{100}{10} \sin(\omega t - 30^\circ).$$

$$\therefore \frac{\sqrt{3}}{T} \int_0^T v_{bc}(t) i_a(t) dt = \sqrt{3} \times \sqrt{3} \times 100 \times 10 \times \cos(60^\circ) \quad \text{Cont.}$$

$$= \boxed{1500} \quad \text{--- (1) mark.}$$

$$Q = 3 \times (V_{an})_{rms} \times (i_a)_{rms} \cdot \sin(30^\circ) = 3 \times 100 \times 10 \times \sin(30^\circ) = 1500 \text{ VAR} \quad \text{--- (1) mark.}$$

17. A single-phase load consumes 5 kW active power and 2 kVAR of reactive power from a 415 V (rms, 50 Hz) terminal. A capacitor C is to be connected in parallel to the load to improve the power factor. Find the value of C required to improve the power factor to 0.95 (lead). 3 marks

$$S = P + jQ, \quad \tan(\theta) = Q/P.$$

After correction, $S_1 = P + jQ_1$, $\tan(\theta_1) = \frac{Q_1}{P}$.


$$\theta = \tan^{-1}(2/5) = 21.801^\circ.$$

$$\theta_1 = -\cos^{-1}(0.95) = -18.19^\circ. \quad \text{--- (2 marks)}$$


$$Q_c = Q - Q_1 = 3.643 \text{ kVAR.}$$

$$Q_c = \omega C V^2 \Rightarrow C = Q_c / \omega V^2 = \frac{3.643 \times 10^3}{2\pi \times 50 \times 415^2} = 67.33 \mu\text{F} \quad \text{--- (1 mark)}$$

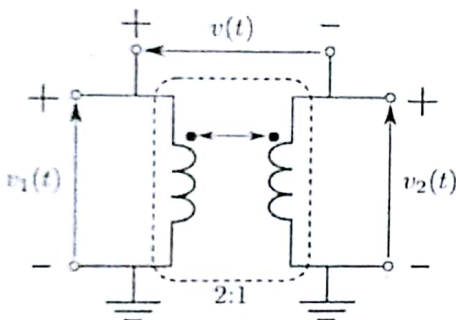18. An ideal transformer has a turns ratio of 2:1 as shown in Figure 8. If the primary winding is excited with $v_1(t) = \sqrt{2} \times 50 \sin(2\pi \times 50t)$ V, find the expressions of the secondary voltage $v_2(t)$ and the voltage $v(t)$ for both the connections as shown in Figure 8a and Figure 8b. 4 marks



(a) Configuration 1

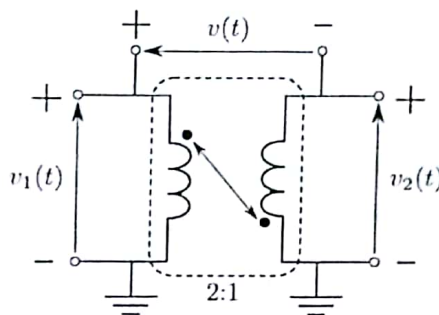

(b) Configuration 2

Figure 8: Circuits for Problem 18

$$v_1(t) \quad N_1 \quad |$$

19. For the circuit shown in Figure 9, the transfer function of the individual blocks are $G_A(j\omega)$ and $G_B(j\omega)$. Find the transfer function $\frac{V_{out}(j\omega)}{V_{in}(j\omega)}$. 2 marks

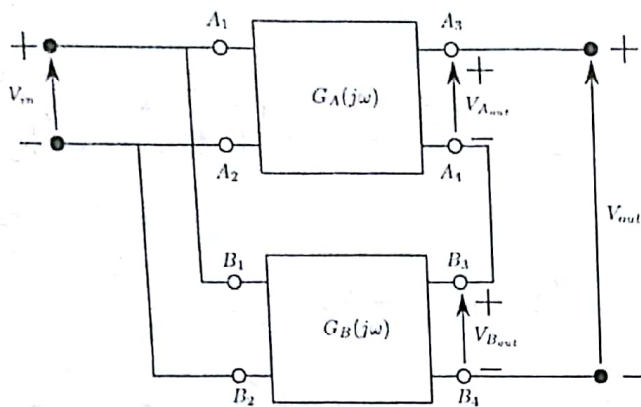



Figure 9: Circuit for Problem 19

$$\frac{V_{Aout}(j\omega)}{V_{in}(j\omega)} = G_A(j\omega)$$

$$\frac{V_{Bout}(j\omega)}{V_{in}(j\omega)} = G_B(j\omega)$$

$$V_{out}(j\omega) = V_{Aout}(j\omega) + V_{Bout}(j\omega) = [G_A + G_B](j\omega) V_{in}(j\omega)$$

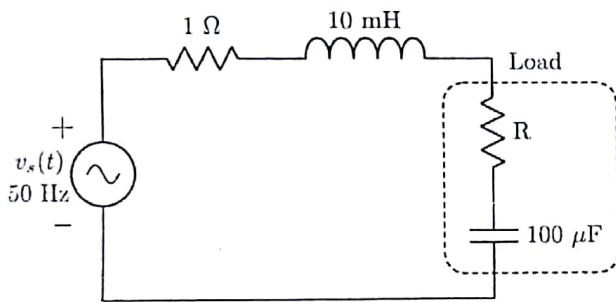20. For the circuit shown in Figure 10, find the value of R such that maximum power is transferred to the load (shown as dotted block in Figure 10) when the source frequency is 50 Hz. 3 marks



$$I_{rms} = \frac{V_s}{\sqrt{(R_s + R)^2 + (X_L - X_C)^2}}$$

$$P_L = I_{rms}^2 R$$

Figure 10: Circuit for Problem 20

$$\frac{\partial P_L}{\partial R} = 0 \Rightarrow R = \sqrt{R_s^2 + (X_L - X_C)^2} \text{ for max } P_L$$

For max Q_L , since C is fixed, $Q_L = I_{rms}^2 X_C$ is max when I_{rms} is max. So, I_{rms} will be max when $R = 0$.

For max $Q_L \Rightarrow R = 0$.

$$S = I_{rms}^2 Z$$

$$S = \frac{V_s^2}{(R_s + R)^2 + (X_e)^2} \cdot \sqrt{R^2 + X_c^2} \quad X_e = X_L - X_C$$

$$\frac{\partial S}{\partial R} = 0 \Rightarrow R = \sqrt{R_s^2 + X_e^2} \quad \text{The End.}$$

Solving for R , we shall get R required for max S .

$$\frac{V_{out}(j\omega)}{V_{in}(j\omega)} = G_A(j\omega) + G_B(j\omega)$$

(2) marks

$$S = \frac{V_s^2}{(R_s + R)^2 + (X_s - X_c)^2} \cdot \sqrt{R^2 + X_c^2}$$

$$\frac{\partial S}{\partial R} = 0$$

$$\Rightarrow [(R_s + R)^2 + X_c^2] \cdot \frac{1}{2\sqrt{R^2 + X_c^2}} \cdot 2R - \sqrt{R^2 + X_c^2} \cdot 2(R_s + R) = 0.$$

$$[(R_s + R)^2 + X_c^2] \cdot R = 2(R^2 + X_c^2)(R_s + R).$$

$$2R_s R + R_s^2 R + R^3 + X_c^2 R = 2R^2 R_s + 2R^3 + 2X_c^2 R_s + 2X_c^2 R.$$

$$R^3 + (2X_c^2 - X_c^2 - R_s^2)R + 2X_c^2 R_s = 0.$$

$$\text{Solving } R = 0.8407 \pm j 34.7 \Omega, -1.6815 \Omega.$$